### Design, implementation of N bit UP/DOWN Counter

### Verilog code

```
module nbud #(parameter N=8)(input clk,rst,swi,output[N-1:0]q);
                                                                Open -
                                                                           B
reg[N-1:0]q;
                                                             module nbud tb();
always @(posedge clk or negedge rst)
                                                             parameter N=8;
                                                             reg clk, rst, swi;
begin
                                                             wire [N-1:0]q;
if(~rst)
                                                             nbud n1(clk,rst,swi,q);
q<=0;
                                                             initial
                                                             begin
else
                                                             clk = 0;
 if(swi==1)
                                                             rst=0;
                                                             swi=0;
 q \le q+1;
                                                             end
 else
                                                             always #5 clk = ~clk;
 q \le q - 1;
                                                             always #100 rst=~rst;
                                                             always #300 swi=~swi;
end
                                                             endmodule
endmodule
```

#### Constraint

```
set sdc version 1.4
current_design nbud

create_clock -name clk -period 500 -waveform {0 1} [get_ports "clk"]
set_clock_transition -rise 0.4 [get_clocks "clk"]
set_clock_transition -fall 0.4 [get_clocks "clk"]
set_input_delay -min 0.2 [get_ports "rst"]
set_input_delay -max 0.4 [get_ports "swi"]
set_load 0.2 [all_outputs]
# set_input_transition 1 [all_inputs]
set_input_transition 1.5 [get_ports "rst"]
set_input_transition 1.5 [get_ports "swi"]
```


# **Optimized Constraint**

```
set_units -capacitance 1000fF
set_units -time 1000ps

# Set the current design
current_design nbud

create_clock -name "clk" -period 500.0 -waveform {0.0 1.0} [get_ports clk]
set_clock_transition 0.4 [get_clocks clk]
set_load -pin_load 0.2 [get_ports {q[7]}]
set_load -pin_load 0.2 [get_ports {q[6]}]
set_load -pin_load 0.2 [get_ports {q[5]}]
set_load -pin_load 0.2 [get_ports {q[4]}]
set_load -pin_load 0.2 [get_ports {q[2]}]
set_load -pin_load 0.2 [get_ports {q[1]}]
set_load -pin_load 0.2 [get_ports {q[1]}]
set_load -pin_load 0.2 [get_ports {q[0]}]
set_input_delay -add_delay -min 0.2 [get_ports rst]
set_input_transition 1.0 [get_ports rst]
set_input_transition 1.5 [get_ports swi]
set_wire_load_mode "enclosed"
```

#### Report on area

 


## Report on power

Open ▼ 🖪	<pre>nbud_power.rep ~/harsha/synthesis/logisyn/output/nbitud1</pre>				
Instance: /nbud					
Power Unit: W					
PDB Frames: /st	im#0/frame#0				
Catagory	Lookaga	Totornal	Cuitchina	To+-1	Row%
Category	Leakage	Internal	Switching	Total	Rowa
memory	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
register	2.84842e-09	1.72832e-07	3.56543e-07	5.32224e-07	91.70%
latch	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
logic	2.28058e-09	3.19358e-08	6.19873e-09	4.04151e-08	6.96%
bbox	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
clock	0.00000e+00	0.00000e+00	7.77600e-09	7.77600e-09	1.34%
pad	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pm	0.00000e+00	0.0000e+00	0.00000e+00	0.00000e+00	0.00%
Subtotal	5.12900e-09	2.04768e-07	3.70518e-07	5.80415e-07	100.00%
	0.88%	35.28%	63.84%	100 00%	100.00%

### Report on timing

```
0 ========
      File
       Edit
               View
  Module:
                               nbud
  Operating conditions:
                               slow (balanced tree)
  Wireload mode:
                               enclosed
  Area mode:
                               timing library
______
Path 1: MET (497089 ps) Setup Check with Pin q reg[7]/CK->D
            Group: clk
      Startpoint: (R) q reg[1]/CK
            Clock: (R) clk
        Endpoint: (R) q reg[7]/D
            Clock: (R) clk
                        Capture
                                         Launch
         Clock Edge:+ 500000
        Src Latency:+ 0
Net Latency:+ 0 (I)
                                              0 (I)
             Arrival:= 500000
               Setup:- 84
      Required Time:= 499916
       Launch Clock:- 0
           Data Path: - 2826
               Slack:= 497089
# Timing Point Flags Arc Edge Cell Fanout Load Trans Delay Arrival Instance
                                                                  (fF) (ps) (ps) (ps) Location
  q_reg[1]/CK - - R (arrival) 8 - 400 0 0
q_reg[1]/Q - CK->Q R DFFRX2 6 203.5 1541 1172 1172
g821__7410/Y - C->Y F NAND4XL 2 1.5 1308 680 1852
g816__2883/Y - B->Y R NOR2BX1 2 1.7 295 477 2329
g814__7482/Y - B->Y R AND2XL 2 1.7 66 198 2528
g801__8246/Y - B->Y R AND2XL 1 1.1 48 113 2640
g793__4319/Y - B->Y F XNOR2X1 1 0.9 54 138 2778
g791__2398/Y - B1->Y R OAI22X1 1 0.6 223 48 2826
q_reg[7]/D <<< - R DFFRX2 1 - - 0 2826</pre>
                                                                                                      (-,-)
```


# Report on QoR

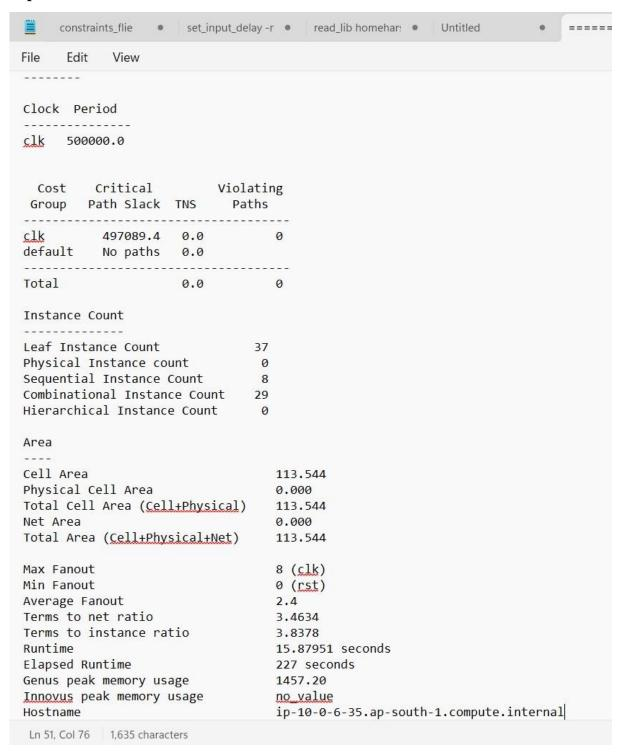

# **Updated Netlist**

```
set_input_delay -r • read_lib homehar: •
                                                            Untitled
     constraints_flie
File
      Edit
             View
module nbud(clk, rst, swi, q);
  input clk, rst, swi;
  output [7:0] q;
  wire clk, rst, swi;
  wire [7:0] q;
  wire UNCONNECTED, UNCONNECTED0, UNCONNECTED1, UNCONNECTED2,
       UNCONNECTED3, UNCONNECTED4, UNCONNECTED5, n_1;
  wire n 2, n 4, n 5, n 6, n 7, n 8, n 9, n 10;
  wire n_11, n_12, n_14, n_15, n_16, n_17, n_18, n_19;
  wire n_20, n_21, n_22, n_24, n_25, n_26, n_27, n_28;
  wire n 29, n 31, n 32, n 37, n 38;
  DFFRX2 \q reg[7] (.RN \q rst), .CK \q clk), .D \q n_32), .Q \q [7]), .QN
       (UNCONNECTED));
  DFFRX2 \q reg[6] (.RN (rst), .CK (clk), .D (n_31), .Q (q[6]), .QN
       (UNCONNECTEDØ));
  OAI22X1 g791 2398(.A0 (swi), .A1 (n_28), .B0 (n_29), .B1 (n_27), .Y
       (n 32));
  OAI22X1 g794 5107(.A0 (swi), .A1 (n 26), .B0 (n 29), .B1 (n 22), .Y
       (n 31));
  DFFRX2 \q reg[5] (.RN (rst), .CK (clk), .D (n 24), .Q (q[5]), .QN
       (UNCONNECTED1));
  DFFRX2 \q reg[3] (.RN (rst), .CK (clk), .D (n_38), .Q (q[3]), .QN
       (UNCONNECTED2));
  XNOR2X1 g795_6260(.A (q[7]), .B (n_25), .Y (n_28));
  XNOR2X1 g793 _4319(.A (q[7]), .B (n_17), .Y (n_27));
  AOI21XL g797_8428(.A0 (q[6]), .A1 (n_20), .B0 (n_25), .Y (n_26));
  OAI22X1 g799 5526(.A0 (<u>swi</u>), .A1 (n 18), .B0 (n 29), .B1 (n 15), .Y
       (n 24));
  DFFRX2 \q reg[2] (.RN (rst), .CK (clk), .D (n_21), .Q (q[2]), .QN
       (UNCONNECTED3));
  DFFRX2 \q reg[4] (.RN (rst), .CK (clk), .D (n_19), .Q (q[4]), .QN
       (UNCONNECTED4));
  XNOR2X1 g798_3680(.A (q[6]), .B (n_16), .Y (n_22));
  XNOR2X1 g812_1617(.A (q[2]), .B (n_12), .Y (n_21));
  NOR2X1 g802_2802(.A (q[6]), .B (n_20), .Y (n_25));
  XNOR2X1 g804_1705(.A (q[4]), .B (n_7), .Y (n_19));
  A0I21XL g805_5122(.A0 (q[5]), .A1 (n_9), .B0 (n_14), .Y (n_18));
  AND2XL g801_8246(.A (q[6]), .B (n_16), .Y (n_17));
  XNOR2X1 g808 _7098(.A (q[5]), .B (n_8), .Y (n_15));
  INVX1 g809(.A (n_14), .Y (n_20));
  DFFRX2 \q reg[1] (.RN (rst), .CK (clk), .D (n 6), .Q (q[1]), .QN
In 60 Cold 2 074 characters
```

#### **Schematic**

 

#### Waveform

